

1477/II

B.C.A. (PART-I) 2<sup>nd</sup> Semester Examination-2022

B.C.A.

(Digital Circuit and Logic Design)

Paper : BCA-203

Time : Three Hours]

[Maximum Marks : 70

- Note:** (i) Answer **five** questions in all.
- (ii) Question No. 1 is compulsory.
- (iii) Answer two questions from section A and B each.
- (iv) All question carry equal marks.

1. Answer any **four** parts of the following:

- (a)  $(324)_{10} = (?)_2$
- (b) State De Morgan's theorem
- (c) Briefly explain Universal logic gates
- (d) Using K-Map, solve the following expression:

$$F = \sum_m(2,5,7,8)$$

## Section-A

2. What is full adder? Give its logic realization and truth table.

3. Using Boolean Algebra simplify the following:

$$F = ABCD + ABC + AB + A\bar{B}$$

Implement the simplified function using NAND/  
NOR gates.

4. What is J K flip-flop? Draw its logic circuit, truth table and timing diagram. Explain the operation of J K flip-flop with all input combinations.

5. Using K-map find the simplified SOP from of:

$$F = \sum_m(0,3,12,15) + d(7,11)$$

## Section-B

6. (a) Using Boolean Algebra prove the following: ✓

$$A'BC + AB'C + ABC = AB + BC + CA$$

(b) Define a Microprocessor system. Explain its function.

7. (a) What is multiplexer? Draw  $8 \times 1$  Mux using suitable logic gates.

(b) Draw the diagram of 4-bit parallel adder and explain its working.

8. (a) Convert the following binary number in to equivalent decimal and hexadecimal numbers:

(i)  $(101101.111)_2$

(ii)  $(11011011.011)_2$

(b) What is four variable K-map? Give different simplification rules for it.

9. Write notes on any **two** of the following:

(a) Encoder and Decoder

(b) Architecture of Micro computer

(c) Counter

••••

*L Anand Kumar*

1477/II

**B.C.A. (PART-I) EXAMINATION, 2022-23**

0107

**(Second Semester)**

**Paper : III**

**BCA-203 : Digital Circuit and Logic Design**

**Time : Three Hours]**

**[Maximum Marks : 70**

- Note:** (i) Answer Five Questions in all.  
(ii) Question No.1 is **Compulsory**.  
(iii) Answer remaining **four** questions, selecting two questions from each Section A and B.  
(iv) All questions carry equal marks.

1. Answer all parts of the following :
- (a) What do you mean by basic and universal gate ?
  - (b) What is difference between JK flip flop and SR flip flop ?

- (c) ~~How many  $2 \times 1$  Mux~~ will be required to implement  $8 \times 1$  Mux ? Explain.
- (d) What is Demorgan's Law ?

### SECTION - A

2. What are SOP and POS form of Boolean expression ? Convert following expression in equivalent POS.

$$F = X'Y'Z + XY'Z' + XYZ$$

3. What is K-map ? Give K-map for four variable.

Simplify the following Boolean function in K-map.

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

4. Explain Binary, Octal and Hexadecimal number and find the value of  $x$  in following :

(i)  $(139)_{10} = (x)_2$

(ii)  $(1542)_8 = (x)_2$

(iii)  $(DAD)_{16} = (x)_8$



5. What do you mean by flip-flop ? Explain JK flip-flop with functional table and circuit diagram. Give the characteristics equation also.

### SECTION – B

6. (a) What do you mean by  $r$  and  $(r - 1)$ 's complement of a number where  $r$  is the base of that number.
- (b) Represent the following using 2's complement :
- (i)  $16 + (-24)$
- (ii)  $16 + 24$
7. (a) Convert the decimal number  $3.248 \times 10^4$  to a single precision floating point binary number.
- (b) Implement the following function with NAND gate :

$$F(x, y, z) = \sum (0, 6)$$

8. (a) Implement MOD-7 up counter using D Flip Flop.

(b) What do you mean by BCD code ? Give the procedure for addition and subtraction of BCD number using example.

9. Write notes on any two of the following :

(a) Minterm and Maxterm

(b) ASCII Code

(c) Register

....